

DP=Double Pole Circuit breaker

BT=Battery

Inv= Inverter / UPS

N=Neutral

L=Phase

Inv L=Phase wire from Inverter / UPS

SW=Switch

S=Socket / Outlet


DM= Dimmer Switch


F= Ceiling Fan

ES= Energy Saver Bulb


Red color= For Line or Phase / Battery + terminal

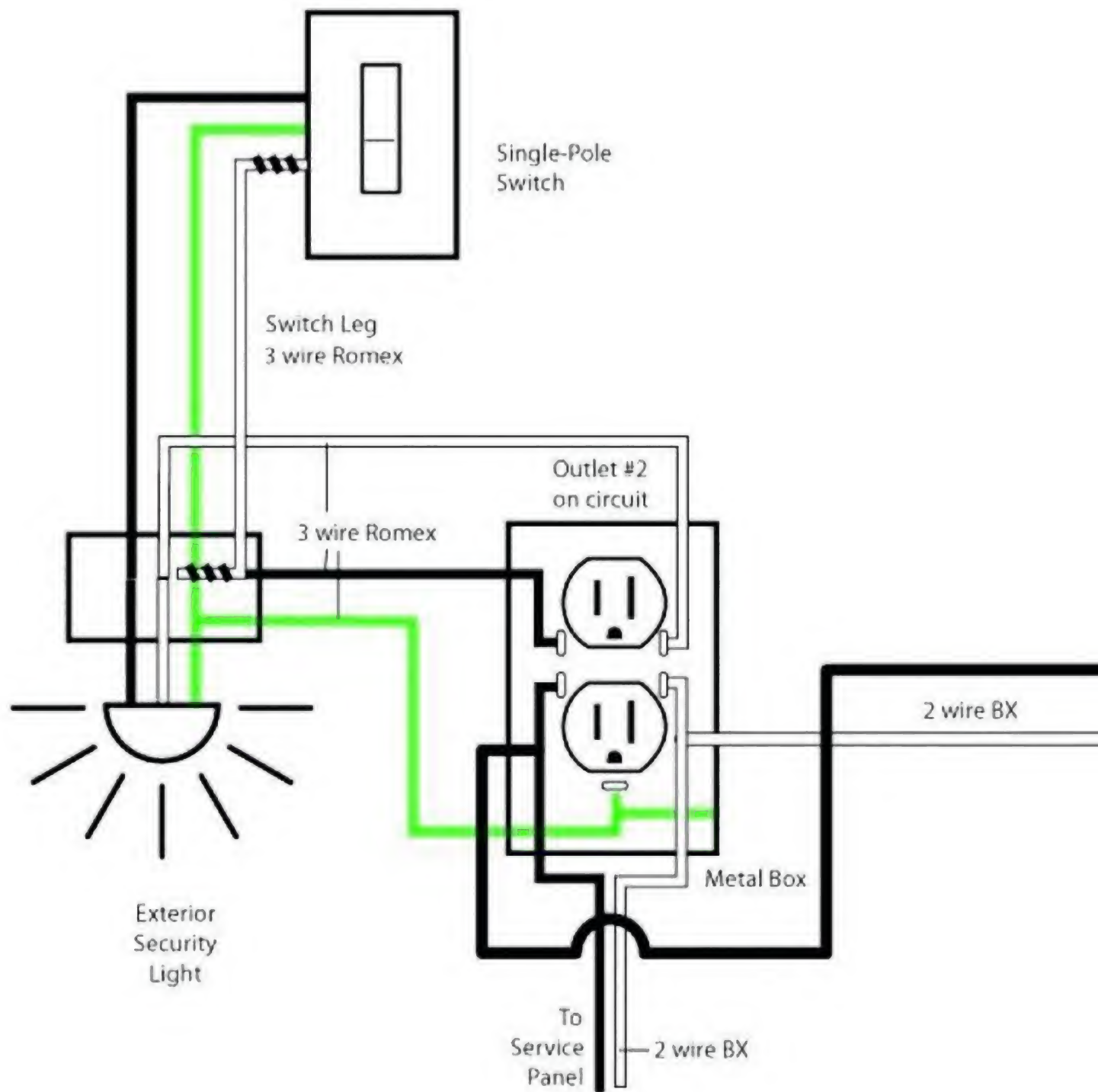Black Color= For Neutral wire / Battery - terminal



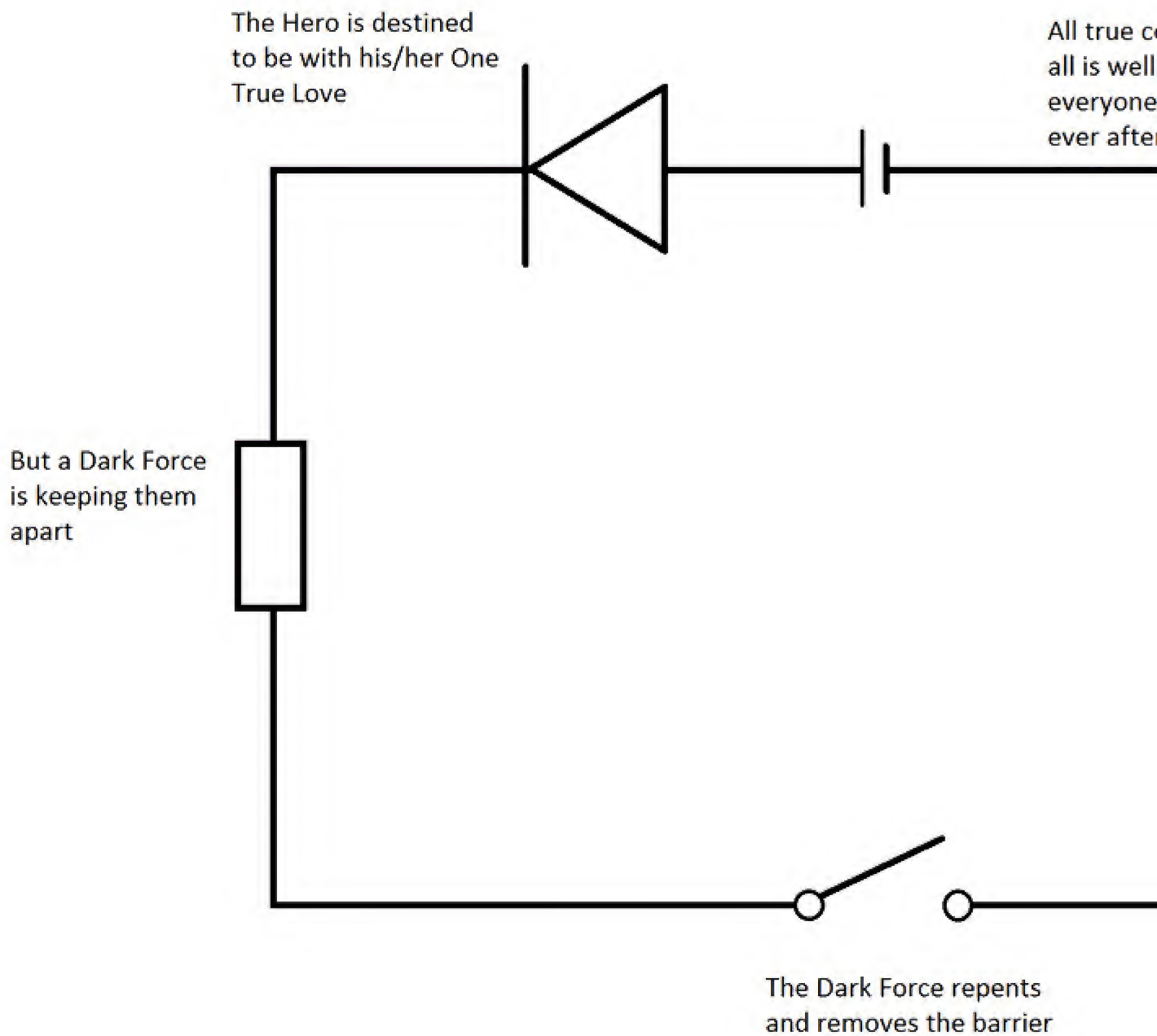

# Basic Electrical Circuit (Dra

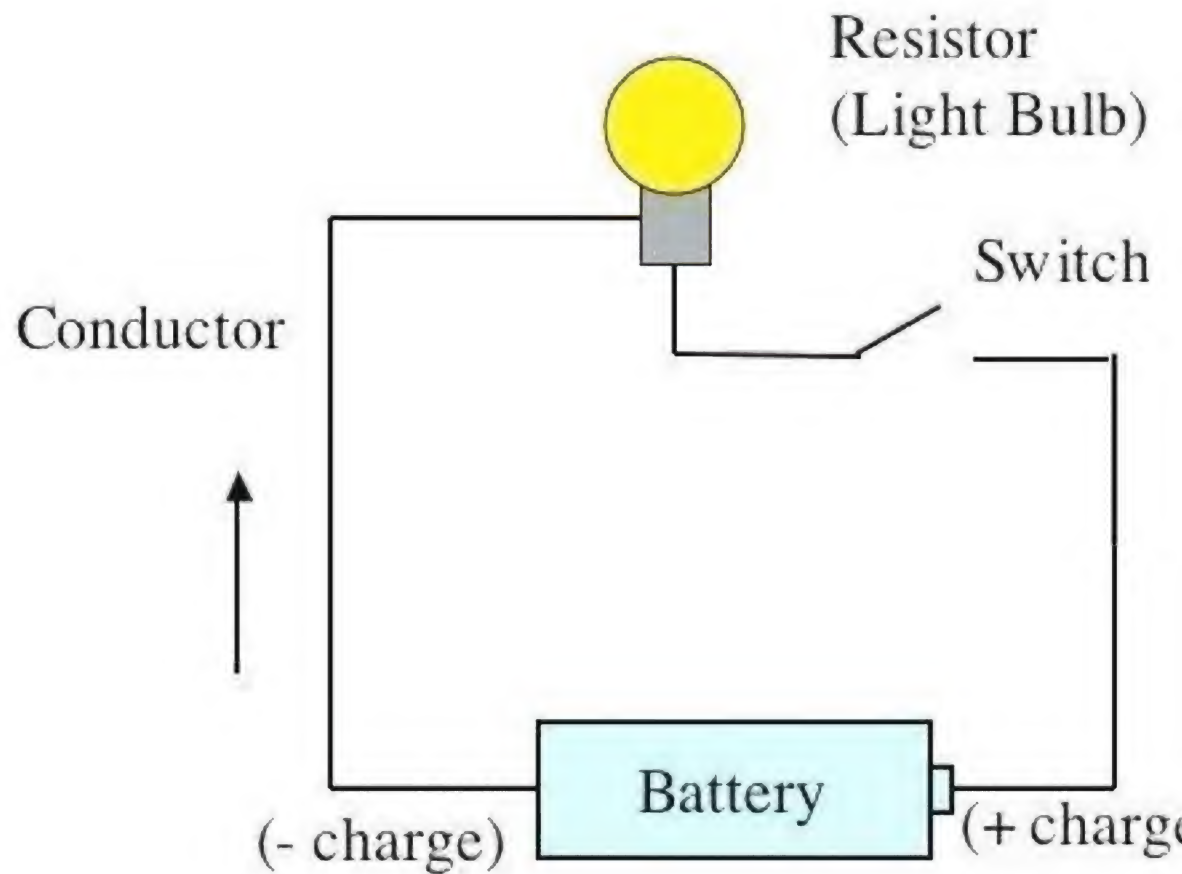

# Simplified "Loop In" wiring (earth omitted for clarity)

